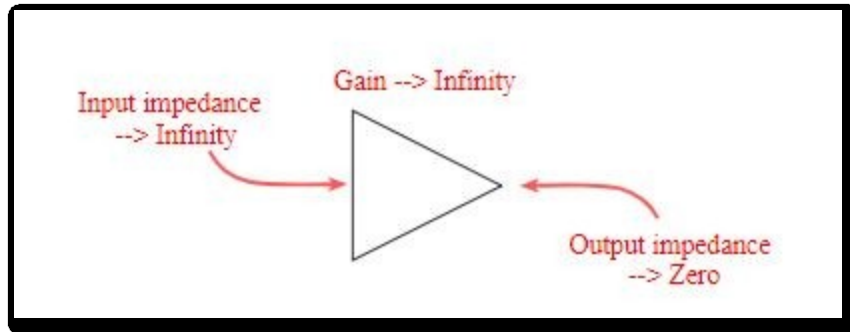


Action of operational amplifier

Operational amplifier characteristics

Operational amplifiers, op-amps have a number of basic features some of which provide advantages, others limit their performance:



Very high gain:

One of the key attributes of operational amplifiers is their very high gain. Typical figures extend from around 10 000 upwards – figures of 100 000 and more are common. Although an open loop amplifier with a level of gain of this order would be of little use, op-amps are able to harness the advantages of the very high gain levels by using negative feedback. In this way the gain levels are very controllable and distortion levels can be kept very low.

The use of negative feedback is key to unlocking the power of operational amplifiers. The high gain of the op-amp combined with clever use of negative feedback means that the negative feedback network is able to control the overall performance of the op-amp circuit block, enables it to perform many different functions.

High input impedance:

High input impedance is another key aspect of op-amps. In theory their input resistance should be infinite, and the op-amps in use today come very close to this with impedances anywhere from 0.25M Ω upwards. Some using MOSFET input stages have an impedance of hundreds of M Ω .

Low output impedance:

The op-amp output impedance is also important. As may be expected this should be low. In the ideal amplifier this should be zero, but in reality many amplifiers have an output impedance of less than a hundred ohms, and many very much less than this. That said, the drive capability of many IC based op-amps is naturally limited.

Common mode rejection:

Another important feature of the op-amp is its common mode rejection. This refers to the situation where the same signal is applied to both inputs. In an ideal amplifier no output should be seen at the output under these circumstances, however the amplifier will never be perfect. The actual common mode rejection ratio, CMMR, is the ratio between the output level when the signal is applied to both inputs compared to the output when it is applied to just one. This figure is expressed in decibels and is typically upwards of 70dB or so.

By using the common mode rejection of an operational amplifier it is possible to design a circuit that reduces the level of interference on a low level signal. The signal and return lines are applied to the two inputs and only differential signals are amplified, any noise or interference picked up and appearing on both lines will be rejected. This is often used within instrumentation amplifiers.

Limited bandwidth:

The bandwidth of an op-amp can vary quite widely. An ideal amplifier would have an infinite bandwidth but as one may imagine this would be impossible create, and also very difficult to use and tame in practise. In reality op-amps have a limited bandwidth. Many of the chips used for audio applications may only exhibit their full gain over a relatively small bandwidth, after this the gain falls. Despite this most circuits act to reduce the gain, and enable this smaller level of gain to be maintained over a larger bandwidth.

Action of operational amplifier continued

Operational amplifiers are linear devices that have all the properties required for nearly ideal DC amplification and are therefore used extensively in signal conditioning, filtering or to perform mathematical operations such as add, subtract, integration and differentiation.

An Operational Amplifier, or op-amp for short, is fundamentally a voltage amplifying device designed to be used with external feedback components such as resistors and capacitors between its output and input terminals. These feedback components determine the resulting function or “operation” of the amplifier and by virtue of the different feedback configurations whether resistive, capacitive or both, the amplifier can perform a variety of different operations, giving rise to its name of “Operational Amplifier”.

An Operational Amplifier is basically a three-terminal device which consists of two high impedance inputs. One of the inputs is called the Inverting Input, marked with a negative or “minus” sign, ($-$). The other input is called the Non-inverting Input, marked with a positive or “plus” sign ($+$).

A third terminal represents the operational amplifiers output port which can both sink and source either a voltage or a current. In a linear operational amplifier, the output signal is the amplification factor, known as the amplifiers gain (A) multiplied by the value of the input signal and depending on the nature of these input and output signals, there can be four different classifications of operational amplifier gain.

Voltage – Voltage “in” and Voltage “out”

Current – Current “in” and Current “out”

Transconductance – Voltage “in” and Current “out”

Transresistance – Current “in” and Voltage “out”


Since most of the circuits dealing with operational amplifiers are voltage amplifiers, we will limit the tutorials in this section to voltage amplifiers only, (V_{in} and V_{out}).

The output voltage signal from an Operational Amplifier is the difference between the signals being applied to its two individual inputs. In other words, an op-amps output signal is the difference between the two input signals as the input stage of an Operational Amplifier is in fact a differential amplifier as shown below.

Differential Amplifier

The circuit below shows a generalized form of a differential amplifier with two inputs marked V_1 and V_2 . The two identical transistors TR_1 and TR_2 are both biased at the same operating point with their emitters connected together and returned to the common rail, $-V_{EE}$ by way of resistor R_E .

Differential Amplifier

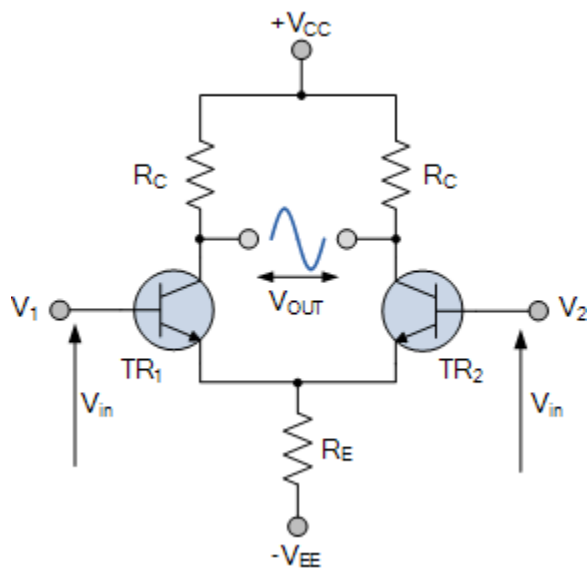

The circuit operates from a dual supply $+V_{CC}$ and $-V_{EE}$ which ensures a constant supply. The voltage that appears at the output, V_{out} of the amplifier is the difference between the two input signals as the two base inputs are in anti-phase with each other.

So as the forward bias of transistor, TR_1 is increased, the forward bias of transistor TR_2 is reduced and vice versa. Then if the two transistors are perfectly matched, the current flowing through the common emitter resistor, R_E will remain constant.

Like the input signal, the output signal is also balanced and since the collector voltages either swing in opposite directions (anti-phase) or in the same direction (in-phase) the output voltage signal, taken from between the two collectors is, assuming a perfectly balanced circuit the zero difference between the two collector voltages.

This is known as the Common Mode of Operation with the common mode gain of the amplifier being the output gain when the input is zero.


Operational Amplifiers also have one output (although there are ones with an additional differential output) of low impedance that is referenced to a common ground terminal and it should ignore any common mode signals that is, if an identical signal is applied to both the inverting and non-inverting inputs there should no change to the output.

However, in real amplifiers there is always some variation and the ratio of the change to the output voltage with regards to the change in the common mode input voltage is called the Common Mode Rejection Ratio or CMRR for short.

Operational Amplifiers on their own have a very high open loop DC gain and by applying some form of Negative Feedback we can produce an operational amplifier circuit that has a very precise gain characteristic that is dependant only on the feedback used. Note that the term “open loop” means that there are no feedback components used around the amplifier so the feedback path or loop is open.

An operational amplifier only responds to the difference between the voltages on its two input terminals, known commonly as the “Differential Input Voltage” and not to their common potential. Then if the same voltage potential is applied to both terminals the resultant output will be zero. An Operational Amplifiers gain is commonly known as the Open Loop Differential Gain, and is given the symbol (A_o).

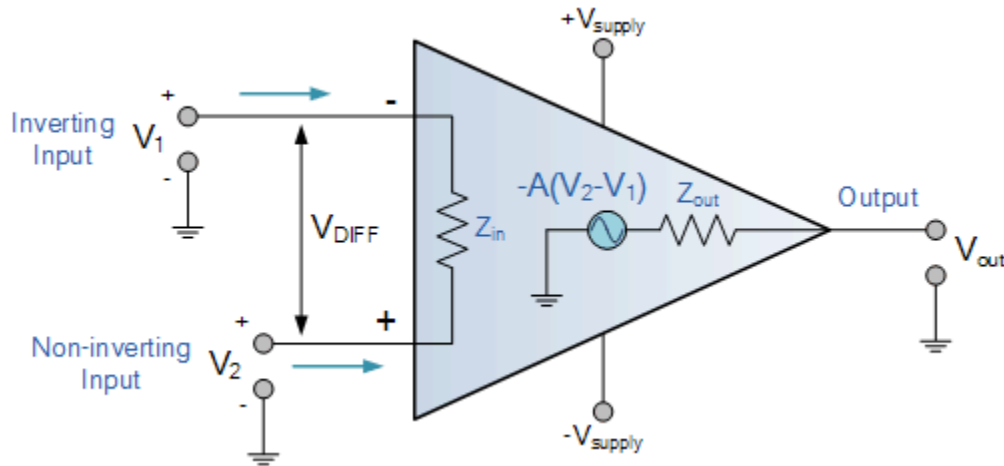Equivalent Circuit of an Ideal Operational Amplifier



Op-amp Parameter and Idealised Characteristic

Open Loop Gain, (A_{vo})

Infinite – The main function of an operational amplifier is to amplify the input signal and the more open loop gain it has the better. Open-loop gain is the gain of the op-amp without positive or negative feedback and for such an amplifier the gain will be infinite but typical real values range from about 20,000 to 200,000.

Input impedance, (Z_{IN})

Infinite – Input impedance is the ratio of input voltage to input current and is assumed to be infinite to prevent any current flowing from the source supply into the amplifiers input circuitry ($I_{IN} = 0$). Real op-amps have input leakage currents from a few pico-amps to a few milli-amps.

Output impedance, (Z_{OUT})

Zero – The output impedance of the ideal operational amplifier is assumed to be zero acting as a perfect internal voltage source with no internal resistance so that it can supply as much current as necessary to the load. This internal resistance is effectively in series with the load thereby reducing the output voltage available to the load. Real op-amps have output impedances in the 100-20k Ω range.

Bandwidth, (BW)

Infinite – An ideal operational amplifier has an infinite frequency response and can amplify any frequency signal from DC to the highest AC frequencies so it is therefore assumed to have an infinite bandwidth. With real op-amps, the bandwidth is limited by the Gain-Bandwidth product (GB), which is equal to the frequency where the amplifiers gain becomes unity.


Offset Voltage, (V_{IO})

Zero – The amplifiers output will be zero when the voltage difference between the inverting and the non-inverting inputs is zero, the same or when both inputs are grounded. Real op-amps have some amount of output offset voltage.

From these “idealized” characteristics above, we can see that the input resistance is infinite, so no current flows into either input terminal (the “current rule”) and that the differential input offset voltage is zero (the “voltage rule”). It is important to remember these two properties as they will help us understand the workings of the Operational Amplifier with regards to the analysis and design of op-amp circuits.

However, real Operational Amplifiers such as the commonly available uA741, for example do not have infinite gain or bandwidth but have a typical “Open Loop Gain” which is defined as the amplifiers output amplification without any external feedback signals connected to it and for a typical operational amplifier is about 100dB at DC (zero Hz). This output gain decreases linearly with frequency down to “Unity Gain” or 1, at about 1MHz and this is shown in the following open loop gain response curve.

Open-loop Frequency Response Curve

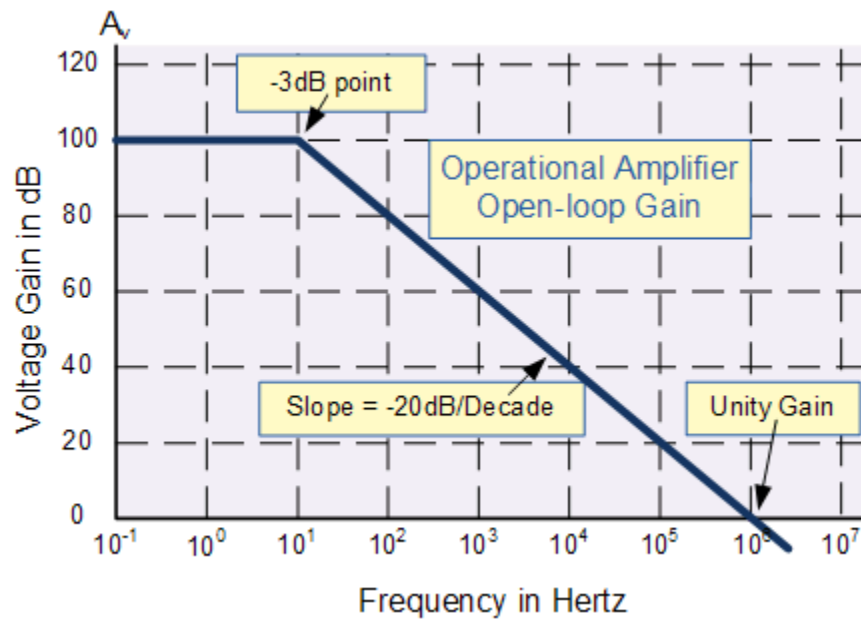

From this frequency response curve we can see that the product of the gain against frequency is constant at any point along the curve. Also that the unity gain (0dB) frequency also determines the gain of the amplifier at any point along the curve. This constant is generally known as the Gain Bandwidth Product or GBP. Therefore:

$$\text{GBP} = \text{Gain} \times \text{Bandwidth} = A \times \text{BW}$$

For example, from the graph above the gain of the amplifier at 100kHz is given as 20dB or 10, then the gain bandwidth product is calculated as:

$$\text{GBP} = A \times \text{BW} = 10 \times 100,000\text{Hz} = 1,000,000.$$

Similarly, the operational amplifiers gain at 1kHz = 60dB or 1000, therefore the GBP is given as:

$$\text{GBP} = A \times \text{BW} = 1,000 \times 1,000\text{Hz} = 1,000,000. \text{ The same!}$$

The Voltage Gain (A_V) of the operational amplifier can be found using the following formula:


$$\text{Op-amp voltage gain } (A_V) = \frac{V_{out}}{V_{in}}$$

and in Decibels or (dB) is given as:

$$20\log(A) \text{ or } 20\log \frac{V_{out}}{V_{in}} \text{ in dB}$$

An Operational Amplifiers Bandwidth

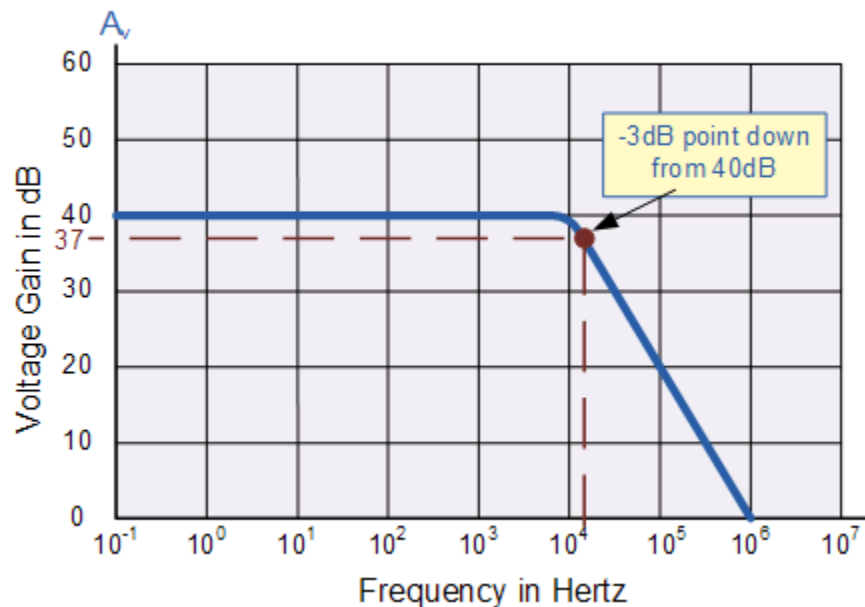The operational amplifiers bandwidth is the frequency range over which the voltage gain of the amplifier is above 70.7% or -3dB (where 0dB is the maximum) of its maximum output value as shown below.



Here we have used the 40dB line as an example. The -3dB or 70.7% of V_{max} down point from the frequency response curve is given as 37dB. Taking a line across until it intersects with the main GBP curve gives us a frequency point just above the 10kHz line at about 12 to 15kHz. We can now calculate this more accurately as we already know the GBP of the amplifier, in this particular case 1MHz.

Operational Amplifier

Example 1.

Using the formula $20 \log (A)$, we can calculate the bandwidth of the amplifier as:

$$37 = 20 \log (A) \quad \text{therefore, } A = \text{anti-log } (37 \div 20) = 70.8$$

$$\text{GBP} \div A = \text{Bandwidth, therefore, } 1,000,000 \div 70.8 = 14,124\text{Hz, or } 14 \text{ kHz}$$

Then the bandwidth of the amplifier at a gain of 40dB is given as 14 kHz as previously predicted from the graph.

Operational Amplifier

Example 2.

If the gain of the operational amplifier was reduced by half to say 20dB in the above frequency response curve, the -3dB point would now be at 17dB. This would then give the operational amplifier an overall gain of 7.08, therefore $A = 7.08$.

If we use the same formula as above, this new gain would give us a bandwidth of approximately 141.2kHz, ten times more than the frequency given at the 40dB point. It can therefore be seen that by reducing the overall “open loop gain” of an operational amplifier its bandwidth is increased and visa versa.

In other words, an operational amplifiers bandwidth is inversely proportional to its gain, ($A \propto 1/\text{BW}$). Also, this -3dB corner frequency point is generally known as the “half power point”, as the output power of the amplifier is at half its maximum value as shown:

$$\text{Power (P)} = \left[\frac{V^2}{R} \right] = [I^2 R]$$

At f_C V or $I = 70.71 \%$ or maximum


If $R = 1$ and V or $I = 0.7071 \text{ max}$

$$\text{Then } P = \left[\frac{[0.7071 \times V]^2}{1} \right] = [(0.7071 \times I)^2 \times 1]$$

Therefore $P = 0.5V$ or $0.5I$ (half power)

Operational Amplifiers Summary


We know now that an Operational amplifiers is a very high gain DC differential amplifier that uses one or more external feedback networks to control its response and characteristics. We can connect external resistors or capacitors to the op-amp in a number of different ways to form basic “building Block” circuits such as, Inverting, Non-Inverting, Voltage Follower, Summing, Differential, Integrator and Differentiator type amplifiers.

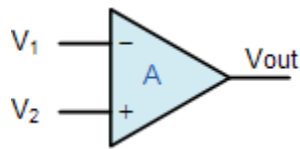

An “ideal” or perfect operational amplifier is a device with certain special characteristics such as infinite open-loop gain A_O , infinite input resistance R_{IN} , zero output resistance R_{OUT} , infinite bandwidth 0 to ∞ and zero offset (the output is exactly zero when the input is zero).

There are a very large number of operational amplifier IC's available to suit every possible application from standard bipolar, precision, high-speed, low-noise, high-voltage, etc, in either standard configuration or with internal Junction FET transistors.

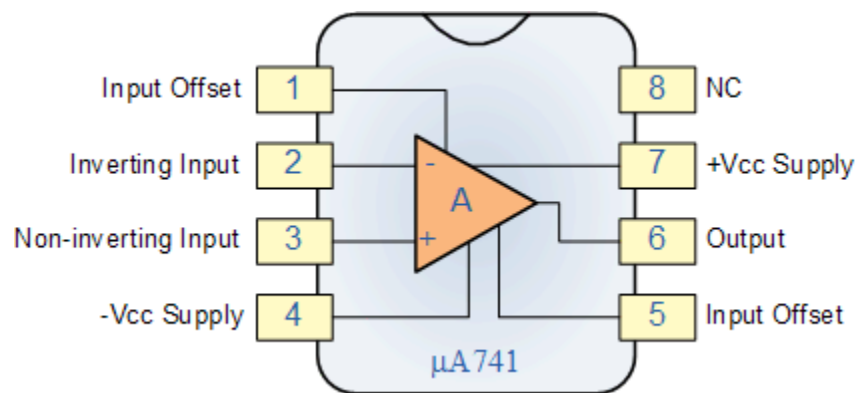Operational amplifiers are available in IC packages of either single, dual or quad op-amps within one single device. The most commonly available and used of all operational amplifiers in basic electronic kits and projects is the industry standard μA -741.



741 operational amplifiers